

Clock-Powered CMOS: A Hybrid Adiabatic Logic Style for Energy-Efficient Computing

Nestoras Tzartzanis and Bill Athas

nestoras@isi.edu, athas@isi.edu

<http://www.isi.edu/acmos>

Information Sciences Institute
University of Southern California




Outline

- The problem
- Standard approaches
- The idea of energy recovery and adiabatic charging
- Driver experiment
- Clock-powered logic
- Conclusions



The Problem

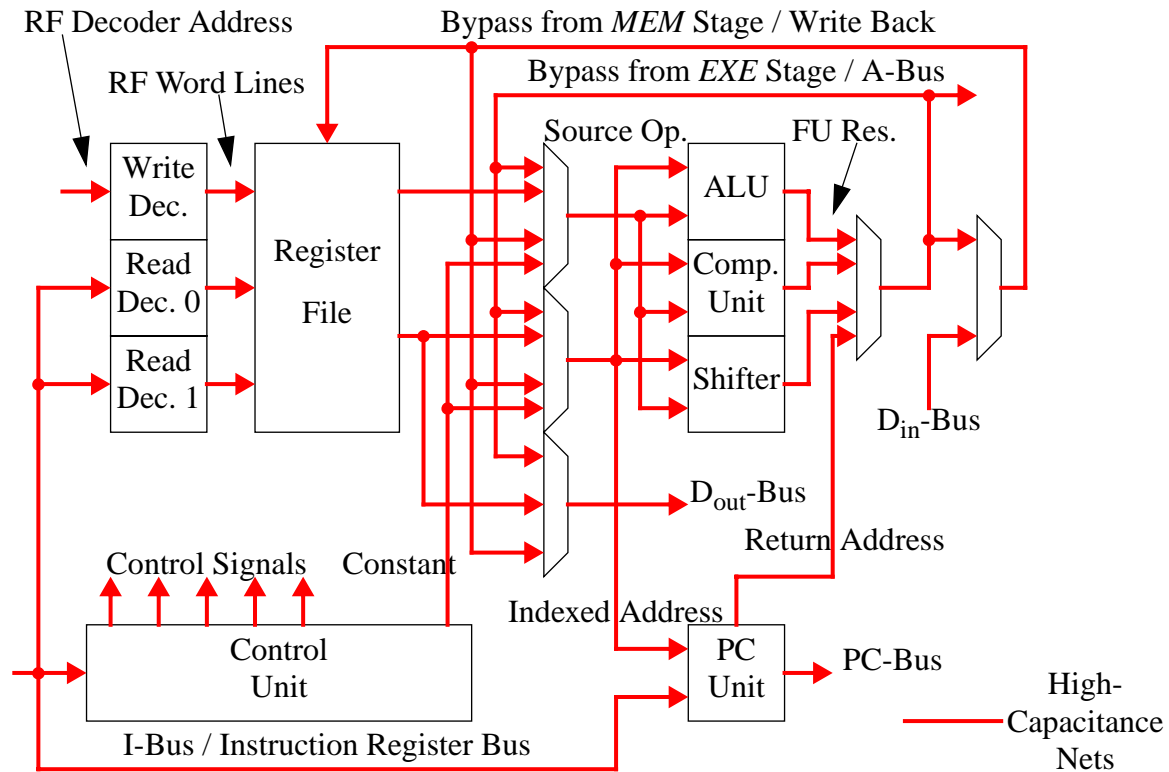


- Processors contain some registers, a little bit of logic, and lots of **long wires**
- Problem: driving **high-capacitance interconnects** in an **energy-efficient** way



A Basic Approach

 - The basic approach in CMOS:
 - Use **reduced-voltage drivers** and **low-to-high voltage converters**





- Approach is limited by threshold voltages



Inverters as Low-Swing Drivers

  - An **inverter** is used as a driver
- A dual-rail-input low-to-high **voltage converter** is used




Driver

- HSPICE simulations for HP $0.5 \mu\text{m}$, 3.3 V process



Energy vs. Delay for the Inverter

 - V_{dd} is set to 3.3 V
- V_{ddL} is varied from 3.3 to 1.1 V
- Record energy for driving the load and delay through the converter




- Voltage reduction is limited by the threshold voltage of the converter
- Delay rapidly increases as V_{ddL} is scaled (3.6 ns for $V_{ddL} = 1.1$ V)




Simple Improvement

 - A modified inverter is used as a driver




Modified Inverter

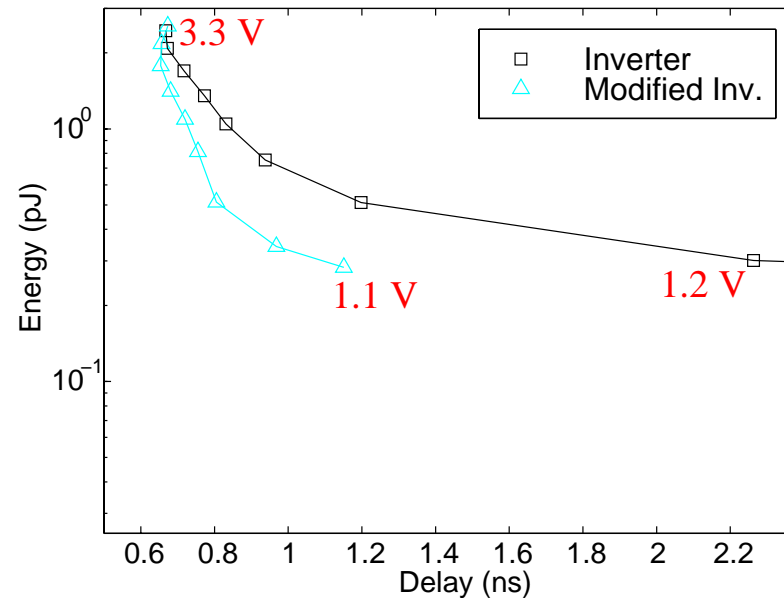

- Reduces delay for low voltages
- Minimum energy dissipation is still limited by the threshold voltage of the converter



Standard CMOS

 


Standard CMOS: $E = CV^2$

- Possible ONLY to reduce voltage



Adiabatic Charging

 


$$\text{Adiabatic CMOS: } E = 2\frac{RC}{T}CV^2$$

- Reduce dissipation by reducing voltage AND increasing the energy transport time



An Adiabatic Driver: The Energy-Recovery Latch

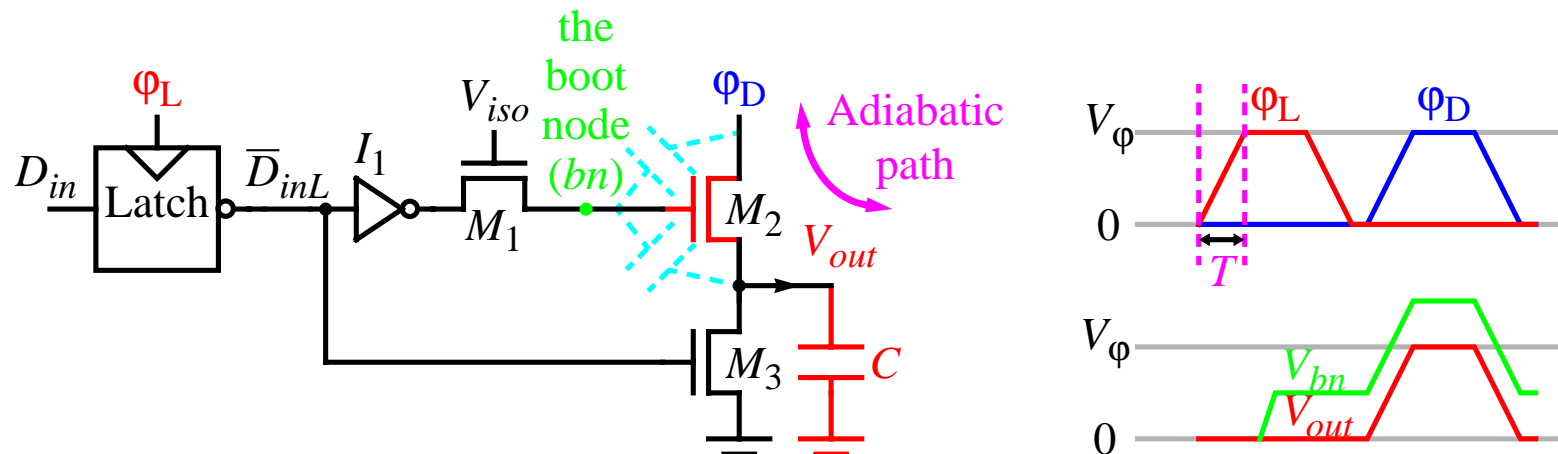- Output node is clock powered
- Energy is injected and recovered through the same path
- Based on bootstrapped clocked buffer [Glasser & Dobberpuhl 1985]




- Minimizes R for given boot-node capacitance
- Operates with two non-overlapping clock phases



Model for On-Resistance of Bootstrapped Transistor

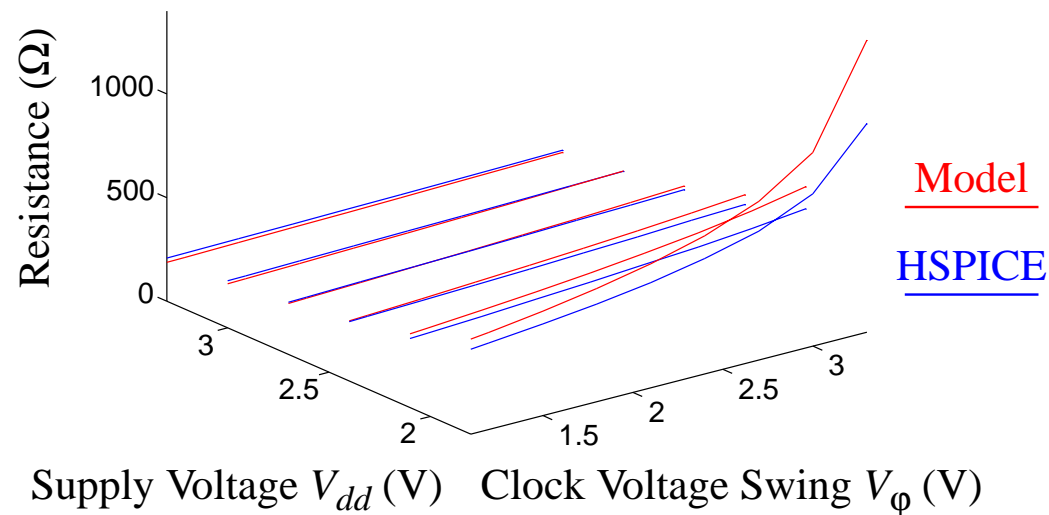- Bootstrap nFET on-resistance was analytically modeled for the case of linear-ramp charging




- Analytical model can be used for sizing bootstrap transistor depending on load capacitance and switching time




Driver Experiment Set-Up

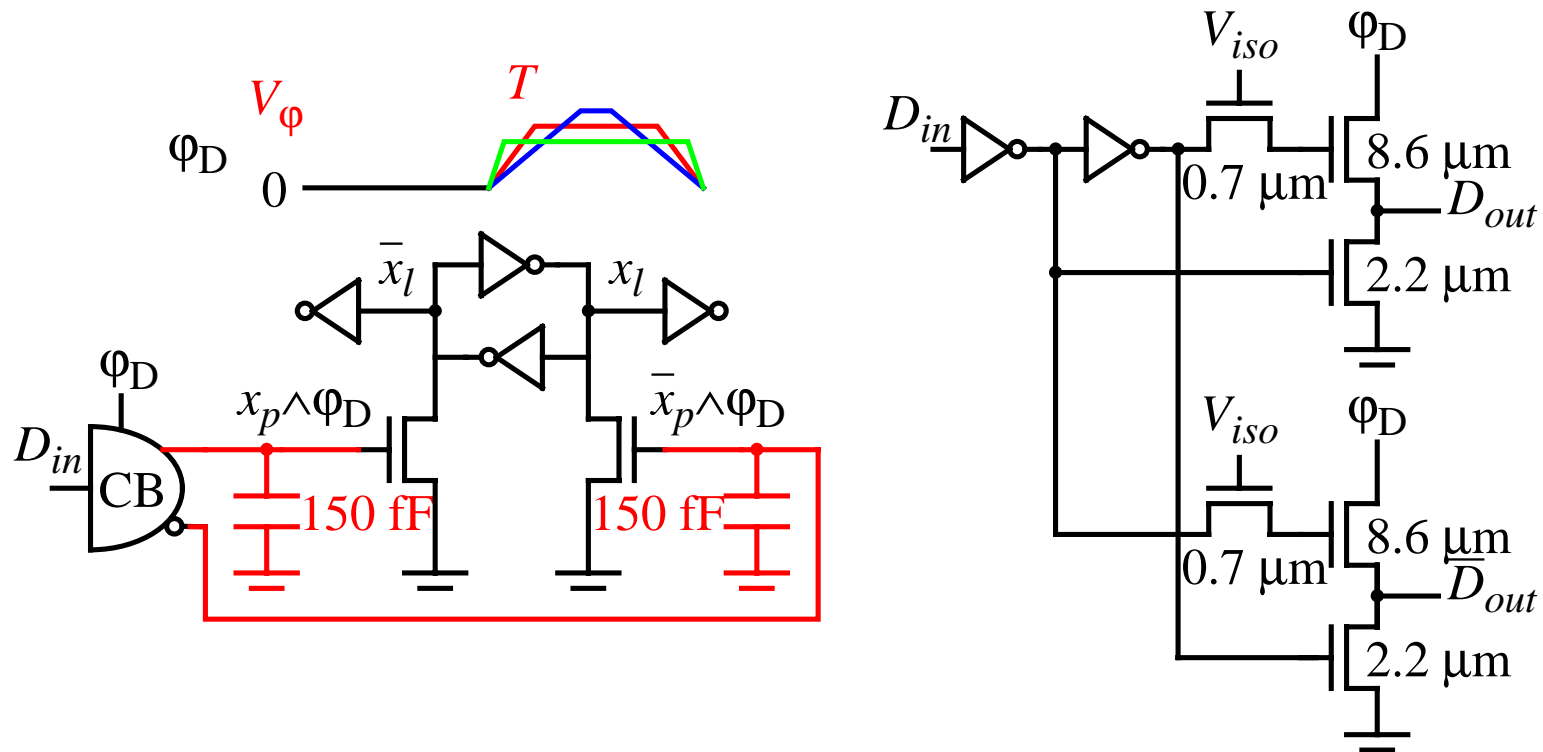- Purpose: to experimentally determine when increasing the switching time T is more energy efficient than reducing the clock voltage swing V_ϕ
- Voltage converter is inherently a pulse-to-level converter



Energy vs. Delay for all Drivers

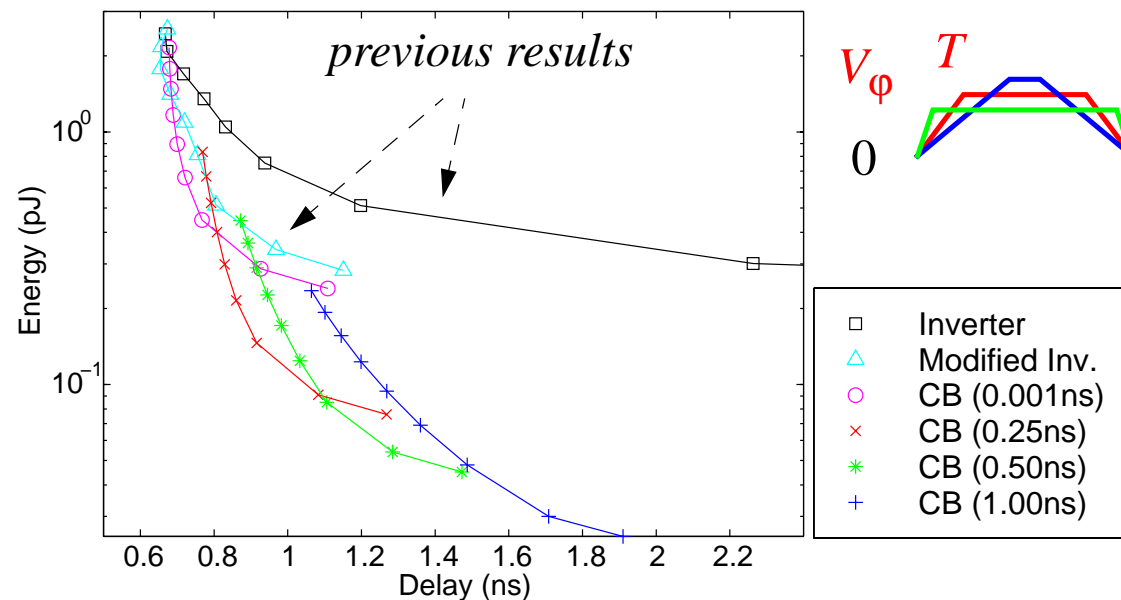- Clock buffer: set V_{ϕ} (3.3-1.1 V) & T (0.001 ns, 0.25 ns, 0.5 ns, 1 ns)
- Conventional drivers: set V_{ddL} (3.3-1.1 V)
- Record energy for driving the load and delay through the converter




- Clock-powered approach has superior scalability because both clock voltage swing V_{ϕ} and switching time T can be varied



Clock-Powered Logic Design

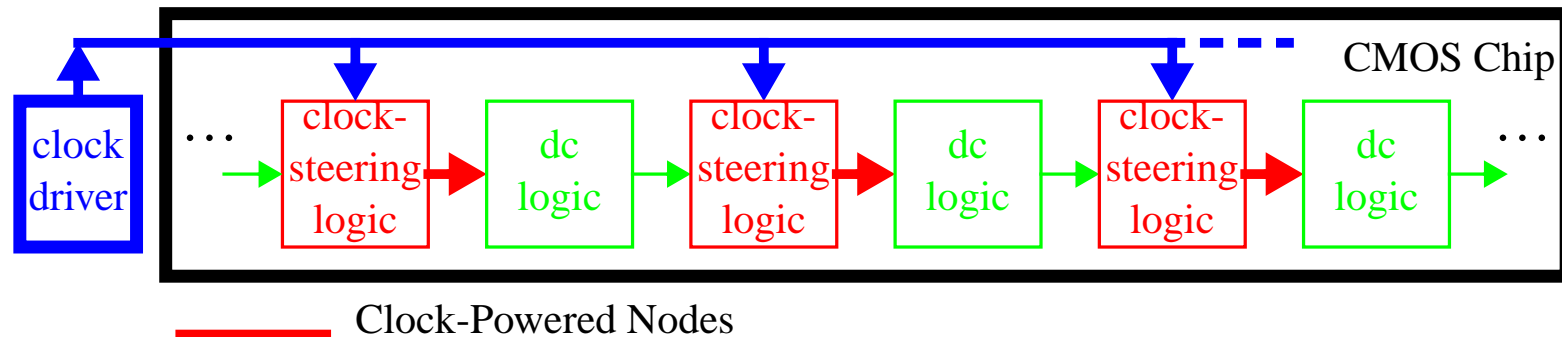- General approach:
 - Use the clock rails to inject and recover the energy
 - Derive as much operating power as possible from the clock rails
- General guidelines:
 - Need an **efficient clock driver**
 - Innovate in the design of a **clock-steering logic**
 - Use conventional **precharged, pass-transistor, static logic**
 - Use the clock-steering logic for high-capacitance loads



Clock-Powered Logic for Optimized Energy vs. Delay

- Reduce dissipation where dissipation is a problem
 - Node-selective energy recovery
 - Energy is recovered only from high-capacitance nodes
- clock-powered nodes: adiabatically switched
 - “1”: pulsed to a clock-voltage swing V_ϕ
 - “0”: clamped at 0 V
- dc-powered nodes: conventionally switched
 - “1”: pulled-up to a voltage V_{dd} from a dc supply
 - “0”: pulled-down to 0 V



The Energy Optimization Problem for Clock-Powered Logic

- Both clock-powered and dc-powered nodes contribute to energy dissipation
- The simplest expression that demonstrates the problem:

$$E = E_{cp} + E_{dc} \sim \frac{RC_{cp}}{T} C_{cp} V_{\phi}^2 + C_{dc} V_{dd}^2$$

- $C_{cp} \gg C_{dc}$ for better energy efficiency
- Asymptotically E_{dc} dominates



Conclusions

- Clocked buffers offer **better energy vs. delay scalability** than reduced-voltage drivers
 - Energy depends on clock voltage swing and transition time
- **Clock-powered logic** is **energy-efficient** for implementing large-scale **microsystems** when:
 - the system can be partitioned into C_{cp} and C_{dc} with effectively $C_{cp} \gg C_{dc}$
 - long transition time of clock-powered nodes can be tolerated without changing overall system delay

